

### Laboratory 3, Total Points: 30


**Due Date: February 21, 2019 (Thursday), 11:59 PM CST**

**Textbook Sections:** Digital Design and Computer Architecture: 3.2, 4.4, and 5.4

In this lab, students will implement a few sequential building blocks of digital systems. Students may refer the above-mentioned textbook sections and Quartus tutorial to complete the lab exercises.

#### Exercises

**1. [7 pts]** A JK flip-flop receives a clock and two inputs, J and K. On the rising edge of the clock, it updates the output, Q. If J and K are both 0, Q retains its old value. If only J is 1, Q becomes 1. If only K is 1, Q becomes 0. If both J and K are 1, Q becomes the opposite of its present state. The toggle (T) flip-flop has a clock, one input, and one output, Q. On each rising edge of the clock, Q toggles to the complement of its previous value. Implement a VHDL module for JK flip-flop and use this module to implement a T flip-flop. Submit VHDL code, simulation results, and synthesized circuits for JK and T flip-flops.

 

**Figure 1: Shift Register**

**2. [8 pts]** A shift register has a clock, a serial input  $S_{in}$ , a serial output  $S_{out}$ , and  $N$  parallel outputs  $Q_{N-1:0}$ , as shown in Figure 1. On each rising edge of the clock, a new bit is shifted in from  $S_{in}$  and all the subsequent contents are shifted forward. The last bit in the shift register is available at  $S_{out}$ . Shift registers can be viewed as serial-to-parallel converters. The input is provided serially (one bit at a time) at  $S_{in}$ . After  $N$  cycles, the past  $N$  inputs are available in parallel at  $Q$ . Implement a generic  $N$ -bit shift register and use it for 4 and 8-bit shift register. Submit VHDL code, simulation results, and synthesized circuits.

**3. [5 points]** An  $N$ -bit Johnson counter consists of an  $N$ -bit shift register with a reset signal. The output of the shift register ( $S_{out}$ ) is inverted and fed back to the input ( $S_{in}$ ). When the counter is reset, all of the bits are cleared to 0. Implement a generic  $N$ -bit Johnson counter and use it for 3 and 5-bit Johnson counter. Submit VHDL code, simulation results, and synthesized circuits.

**4. [10 points]** Gray codes have a useful property in that consecutive numbers differ in only a single bit position. Table 1 lists a 3-bit Gray code representing the numbers 0 to 7. Design a UP/DOWN 3-bit modulo 8 Gray code counter with no inputs and three outputs. When reset, the output should be 000. If  $UP=1$ , the output should advance to the next Gray code on each rising clock edge. After reaching 100, it should repeat with 000. If  $UP = 0$ , the counter retreats to the previous number. Use **if** and **case** structs in VHDL to implement the exercise.

| Number | Gray code |   |   |
|--------|-----------|---|---|
| 0      | 0         | 0 | 0 |
| 1      | 0         | 0 | 1 |
| 2      | 0         | 1 | 1 |
| 3      | 0         | 1 | 0 |
| 4      | 1         | 1 | 0 |
| 5      | 1         | 1 | 1 |
| 6      | 1         | 0 | 1 |
| 7      | 1         | 0 | 0 |

**Table 1: 3-bit Gray Code**